

PHY 108: ELECTRICITY & MAGNETISM

EXPERIMENT 1 : OHM'S LAW

Lab Report:

Date: 27.10.21	
Name of the Students and IDs	(1) Robeya Akter Thabna
	(2) 2013813042
	(3)

#1: Record the data from Table 3-1.

	R ₁			R ₂			R ₃		
	Nominal R: 2.2 kΩ			Nominal R: 4.7 kΩ			Nominal R: 10 kΩ		
	Measured R: 2.16 kΩ			Measured R: 4.67 kΩ			Measured R: 9.9 kΩ		
	Measured Values		I _{Calculated}	Measured Values		I _{Calculated}	Measured Values		I _{Calculated}
	E _{Measured}	I _{Measured}		E _{Measured}	I _{Measured}		E _{Measured}	I _{Measured}	
1 V	1.03 V	0.47 mA	0.45 mA	1.00 V	0.21 mA	0.21 mA	1.00 V	0.10 mA	0.1 mA
2 V	2.04 V	0.94 mA	0.91 mA	2.02 V	0.42 mA	0.40 mA	2.03 V	0.20 mA	0.2 mA
5 V	5.02 V	2.31 mA	2.27 mA	5.00 V	1.07 mA	1.06 mA	4.96 V	0.51 mA	0.5 mA
10 V	10.02 V	4.62 mA	4.55 mA	9.97 V	2.12 mA	2.13 mA	9.97 V	1.02 mA	1.0 mA
15 V	15.02 V	6.96 mA	6.82 mA	15.00 V	3.21 mA	3.19 mA	15.04 V	1.53 mA	1.5 mA
20 V	20.08 V	9.33 mA	9.09 mA	20.06 V	4.27 mA	4.26 mA	20.04 V	2.04 mA	2.0 mA
25 V	25.09 V	11.75 mA	11.36 mA	25.06 V	5.36 mA	5.32 mA	25.01 V	2.55 mA	2.5 mA

#2: Comment on the measured current compared to calculated currents.

For,
R₁

$$I_{\text{Measured}} = 0.94 \text{ mA}$$

$$I_{\text{Calculated}} = 0.91 \text{ mA}$$


$$\therefore \% \text{ of Error} = \left| \frac{I_{\text{Calculated}} - I_{\text{Measured}}}{I_{\text{Calculated}}} \right| \times 100\% = \left| \frac{0.91 - 0.94}{0.91} \right| \times 100\% = 3.3\%$$

So, as calculated all other values of I_{Measured} and $I_{\text{Calculated}}$ the % of error are minimal between measured current and calculated current the error is minimal.

PHY 108: ELECTRICITY & MAGNETISM

EXPERIMENT 1 : OHM'S LAW
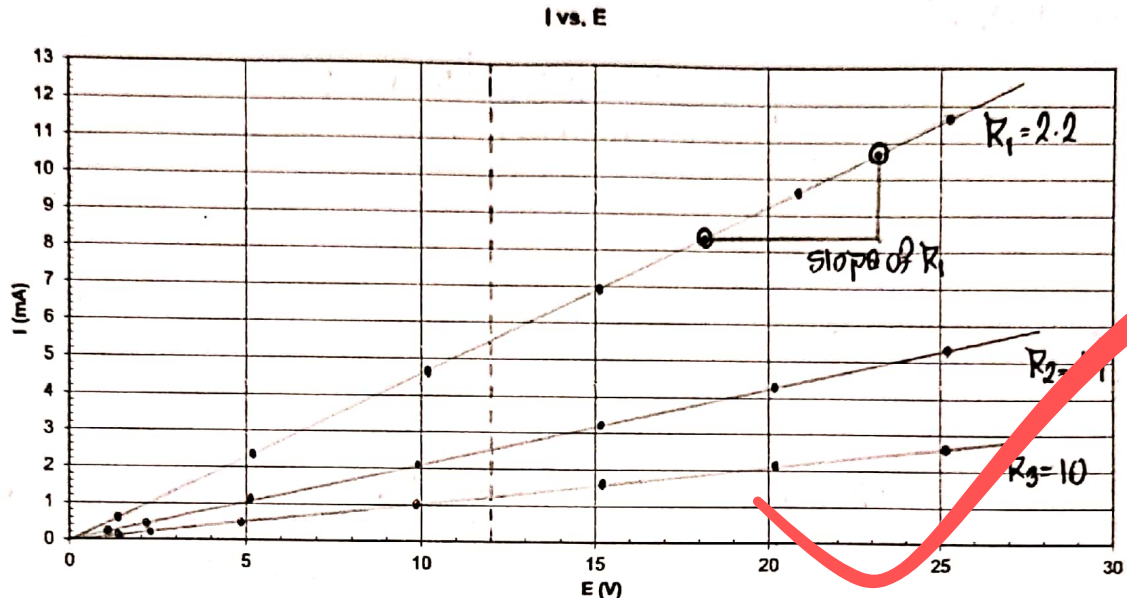
#3: Use the data obtained in Table 3.1 to plot I_{measured} vs. E_{measured} graph.



#4: What does the inverse of the slope of your graphs represent? Illustrate using an example.

The inverse of the slope of my graphs represent the resistance of the resistor.

$$R_1 \text{ Inverse slope} = \frac{\Delta I}{\Delta E} = \frac{I_2 - I_1}{E_2 - E_1} = \frac{10.7 - 8.21}{23 - 18} = 0.408 \text{ K}\Omega^{-1} \text{ or } 0.5 \text{ K}\Omega^{-1}$$

The slope is same as the slope of the curve.

2K Ω

#5: Using your graph, estimate the current that would flow through each resistor at $E = 12$ volts and compare it with the calculated value ($12 \text{ V} / R_{\text{measured}}$). Calculate the error.

For $E = 12 \text{ V}$

Measured Resistance	Estimated Current from Graph	Calculated Current ($12 \text{ V} / R_{\text{measured}}$)	% of Error
$R_1 = 2.16 \text{ K}\Omega$	5.5 mA	5.56 mA	1.08%
$R_2 = 4.67 \text{ K}\Omega$	2.6 mA	2.57 mA	1.17%
$R_3 = 9.82 \text{ K}\Omega$	1.1 mA	1.22 mA	9.84%

$$R_1 \Rightarrow \% \text{ error} = \left| \frac{5.56 - 5.5}{5.56} \right| \times 100\% = 1.08\%$$

$$R_2 \Rightarrow \% \text{ " " } = \left| \frac{2.57 - 2.6}{2.57} \right| \times 100\% = 1.17\%$$

$$R_3 \Rightarrow \% \text{ " " } = \left| \frac{1.22 - 1.1}{1.22} \right| \times 100\% = 9.84\%$$